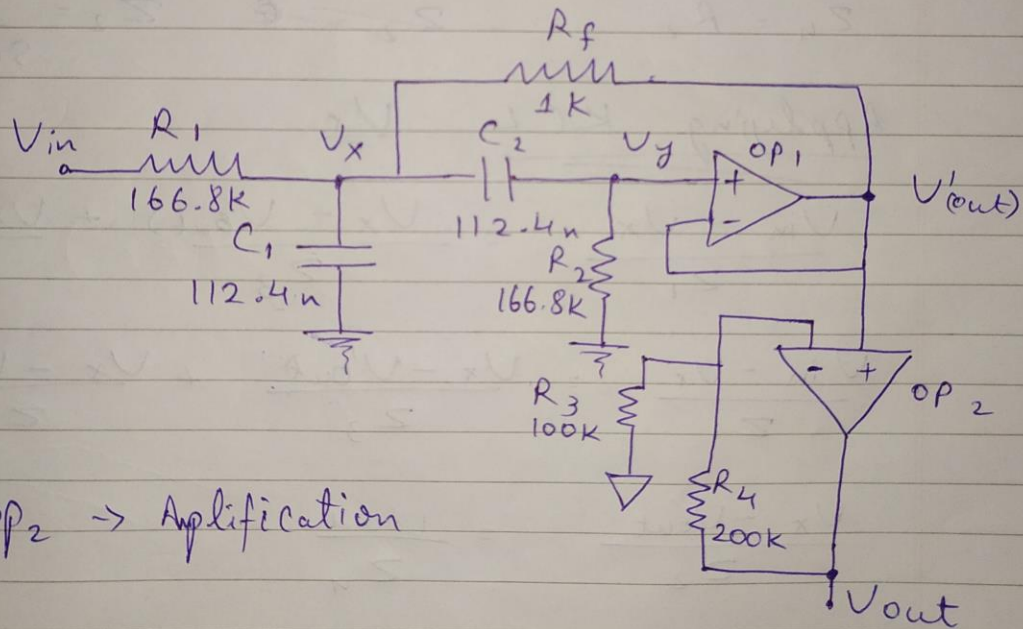


a) I studied different types of band pass filter for my frequency the Sallen key worked best.

In Sallen - key my f_3 & f_5 were already below 0.75V so no need of cascading.



$OP_2 \rightarrow$ Amplification

b) No cascading needed because desired V_{bode} plot i.e. $f_4 \rightarrow$ peak f_3 & f_5 below 0.75 was obtained.

$$c) \quad \begin{array}{lll} Z_1 = R_1 & Z_3 = R_f & \\ Z_4 = R_2 & \cancel{Z_2 = 0} & Z_2 = \frac{1}{sC} \end{array}$$

Applying KCL V_x

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V'_{out}}{Z_3} + \frac{V_x - V_{out}}{Z_2}$$

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V'_{out}}{Z_3} + \frac{V_x - V_{out}}{Z_2}$$

$$\frac{V_x - V_{out}}{Z_2} = \frac{V'_{out}}{Z_4}$$

$$V_x = V'_{out} \left(\frac{Z_2}{Z_4} + 1 \right)$$

$$V_{in} - V_{out} \left(\frac{Z_2}{Z_4} + 1 \right)$$

$$\frac{V_{in} - V'_{out} \left(\frac{Z_2}{Z_4} + 1 \right)}{Z_1} = \frac{V'_{out} \left(\frac{Z_2}{Z_4} + 1 \right) - V'_{out}}{Z_3} + \frac{V'_{out} \left(\frac{Z_2}{Z_4} + 1 \right) - V'_{out}}{Z_2}$$

$$\frac{V'_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

Let $G_1 = 1 + \frac{R_b}{R_a}$

[where in our circuit $R_a \rightarrow \infty$
ie $\frac{R_b}{R_a} = 0$]

On including

R_1, R_2, R_f, C_1, C_2

we get

$$\Rightarrow \frac{\left(1 + \frac{R_b}{R_a} \right) \frac{s}{R_1 C_1}}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{R_b}{R_a R_f C_1} \right) s + \frac{\left(1 + \frac{R_b}{R_a} \right) \frac{s}{R_1 C_1}}{\frac{R_1 + R_f}{R_1 R_2 R_f C_1 C_2}}}$$

Q factor

used for f_o

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{R_f + R_1}{C_1 C_2 R_1 R_2 R_f}} \quad \left[\omega_0^2 = (2\pi f_0)^2 \right]$$

$$Q \text{ factor} = \frac{\sqrt{\frac{R_1 + R_f}{R_1 R_f R_2 C_1 C_2}}}{\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{R_b}{R_a R_b C_1}}$$

$$= \frac{\sqrt{(R_1 + R_f) R_1 R_f R_2 C_1 C_2}}{R_1 R_f (C_1 + C_2) + R_2 C_2 \left(R_f - \frac{R_b R_1}{R_a} \right)}$$

$$\left[\frac{R_b}{R_a} = 0 \right]$$

$$\Rightarrow \frac{\sqrt{(R_1 + R_f) R_1 R_f R_2 C_1 C_2}}{R_1 R_f (C_1 + C_2) + R_2 C_2 (R_f)}$$